
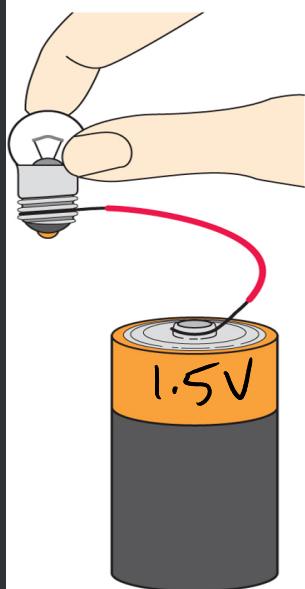


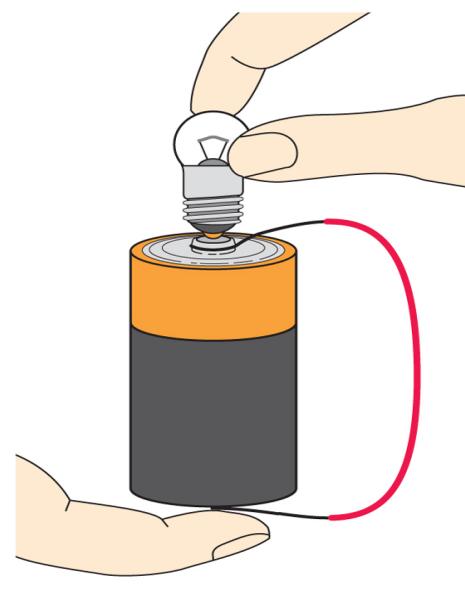
Copyright © McGraw-Hill Education. All rights reserved. No reproduction or distribution without the prior written consent of McGraw-Hill Education.



(a)




(b)

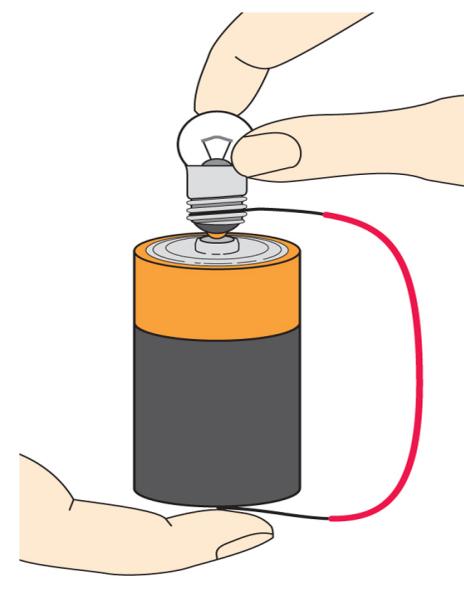


(c)

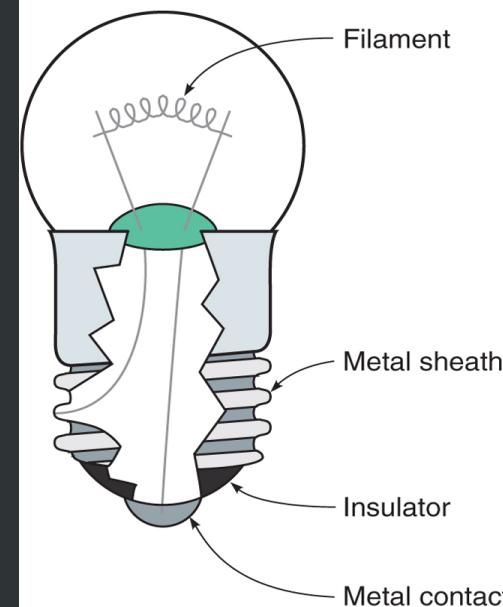Copyright © McGraw-Hill Education. All rights reserved. No reproduction or distribution without the prior written consent of McGraw-Hill Education.



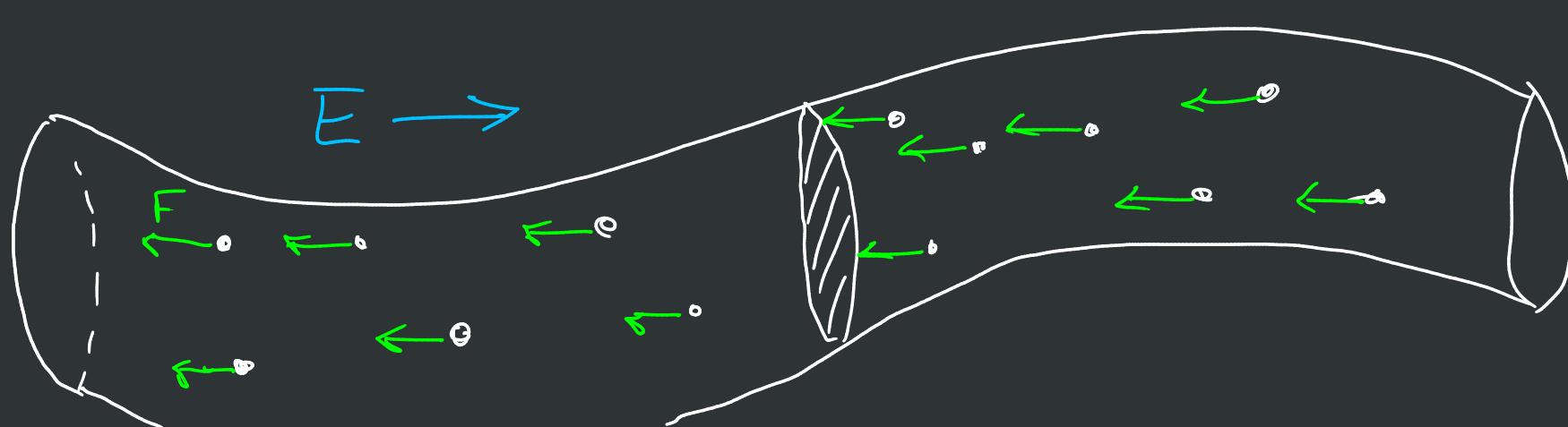Current - measure of the flow of charges through a cross section of wire



Current, I

Current = # of Coulombs of charge that pass a point  
second



$$I = \frac{\Delta q}{t} \quad \left[ \frac{C}{s} \right] \rightarrow \begin{array}{l} [\text{Ampere}] \\ [\text{Amp}] \\ [A] \end{array}$$

$$\rightsquigarrow V = I \cdot R$$

Ohm's Law

$$\text{Resistance} = \frac{\text{Voltage}}{\text{Current}} \rightsquigarrow \boxed{R = \frac{V}{I}} \quad \left[ \frac{\text{Volt}}{\text{Amp}} \right] = [\text{Ohm}] = [Q]$$

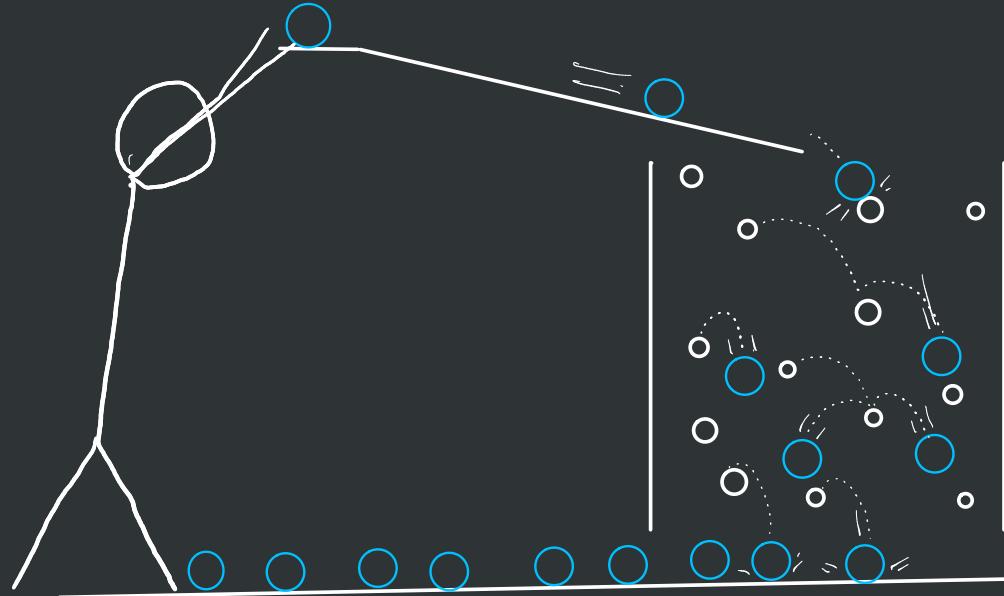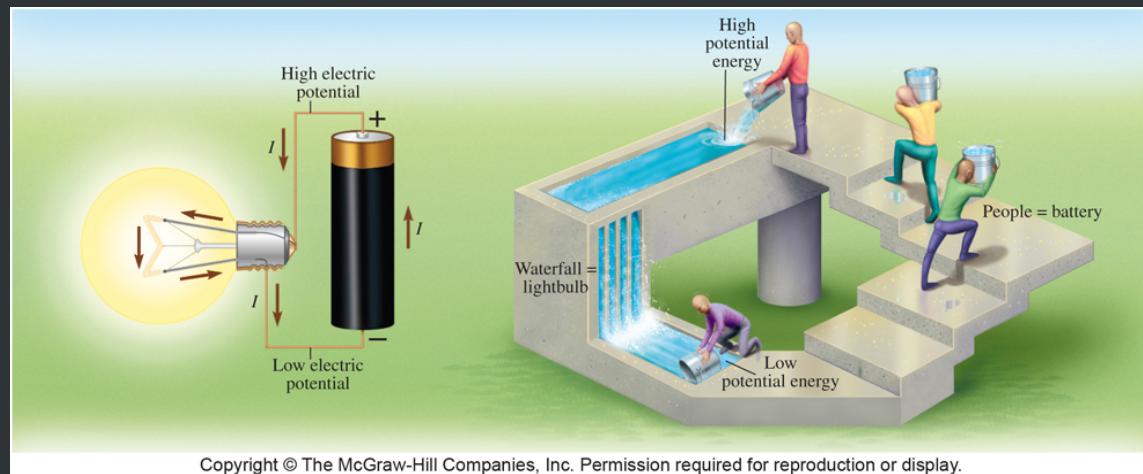resistance  $\rightarrow$  restriction to the flow of charges.




→ 12 Volt battery



→ Resistance  $\rightarrow \underline{80\Omega}$

→ Current = ?
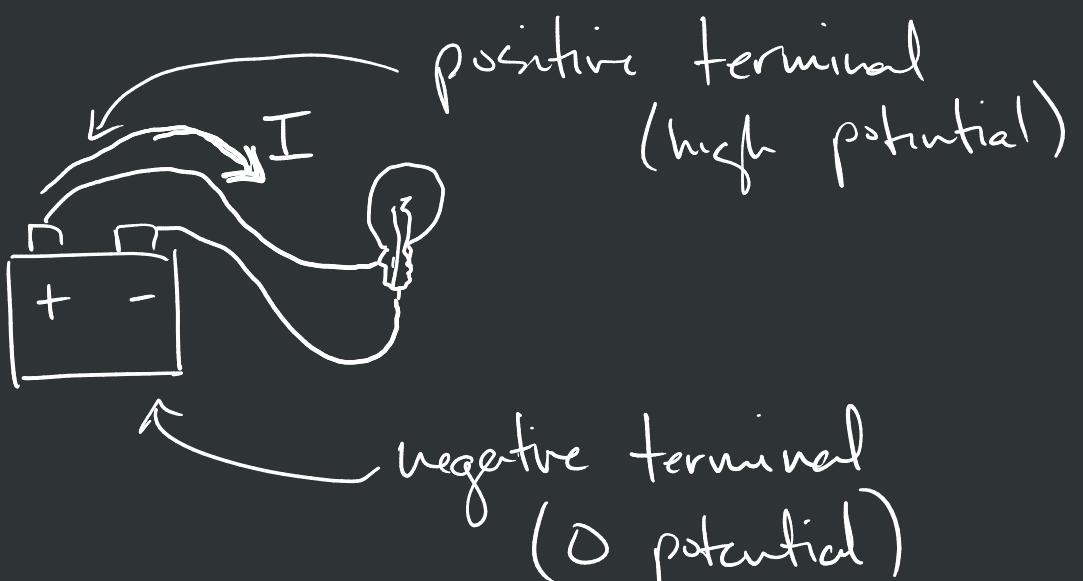
$$I = \frac{V}{R} = \frac{12V}{80\Omega} = 0.15A$$




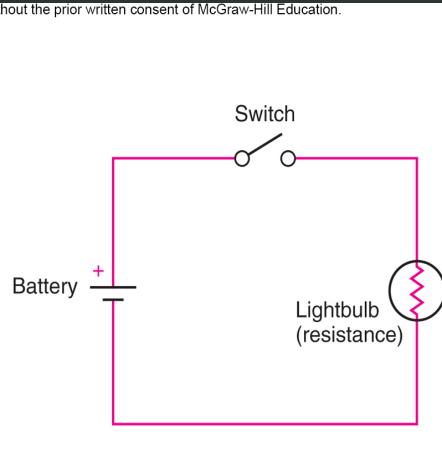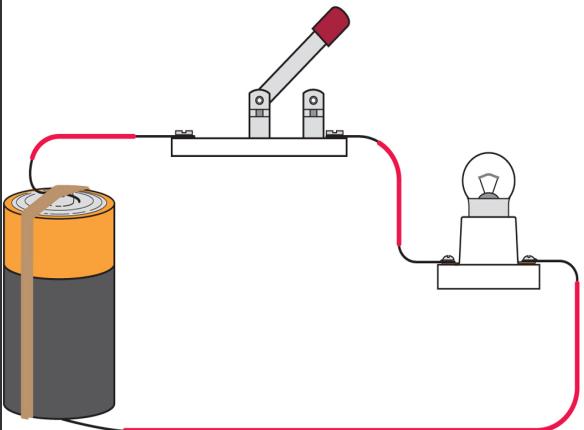Conventional current,  $I$ ,  
flows from  $(+)$  to  $(-)$   
terminals



lightbulbs

## Resistors in Series

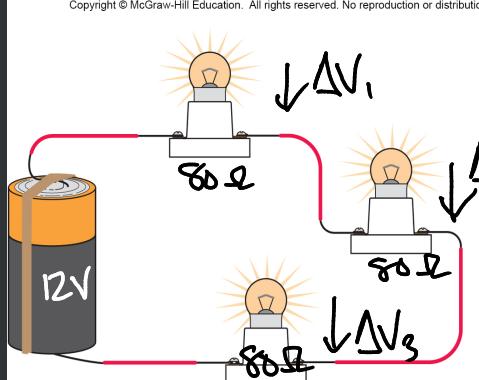

$$\Delta V_{\text{battery}} - \Delta V_1 - \Delta V_2 - \Delta V_3 = 0$$


} add up to find the equivalent resistance

$$R_E = R_1 + R_2 + R_3 + \dots$$

$$\hookrightarrow R_E = 240\Omega = 80 + 80 + 80$$

$$I = \frac{12V}{240\Omega} = .05A$$

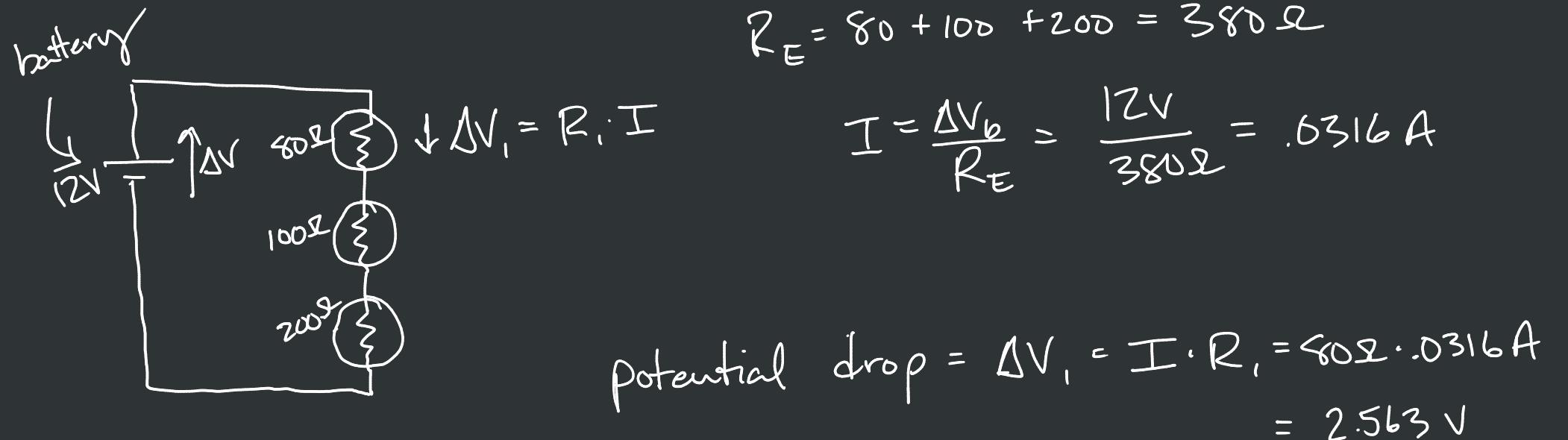
$$I_{R_E} = \frac{V}{R_E} \quad \leftarrow \text{Ohm's Law}$$



$$\Delta V_2 = I R_2 = 3.16 V$$

$$\Delta V_3 = I R_3 = 6.32 V$$

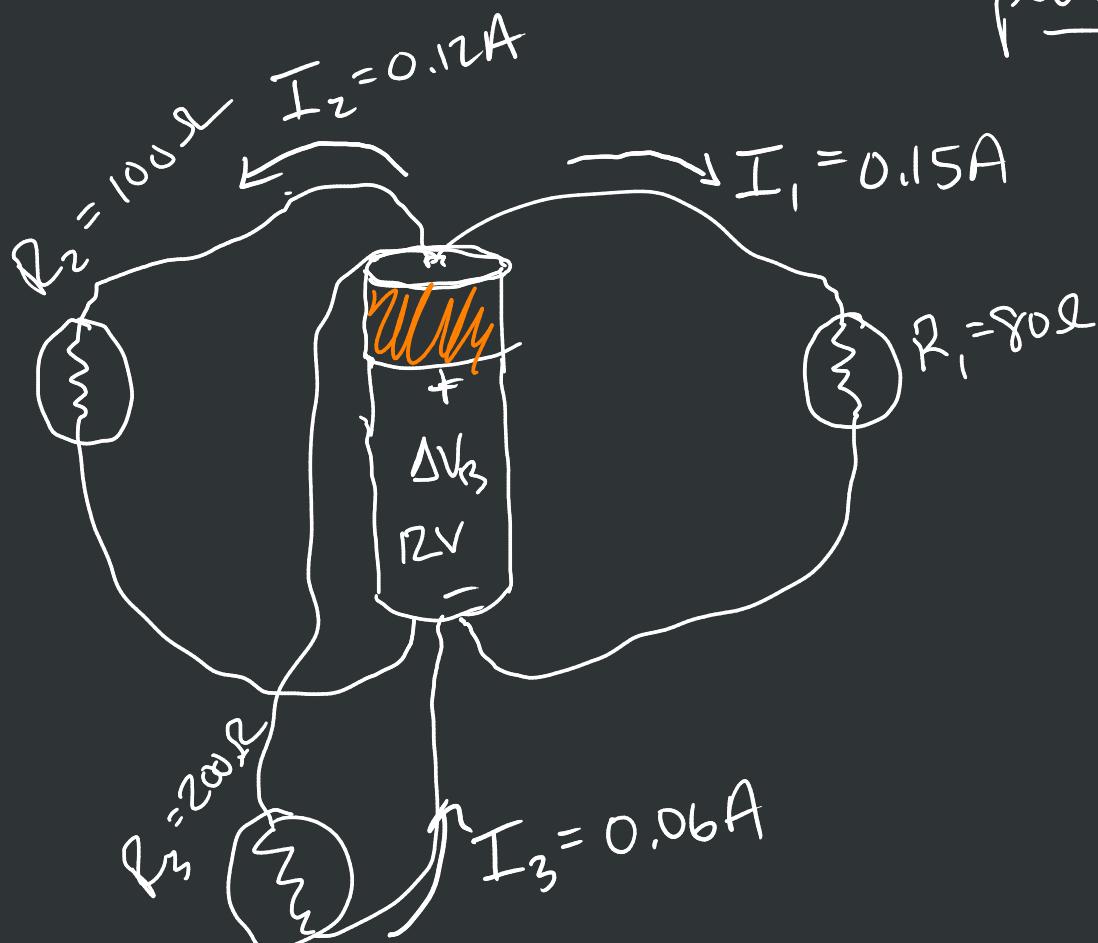
Resistors in parallel  $\rightarrow$  each device has its own connection to the power source.



$$I_1 = \frac{V}{R_1} = \frac{12V}{80\Omega} = 0.15A$$

$$I_2 = \frac{V}{R_2} = \frac{12V}{100\Omega} = 0.12A$$
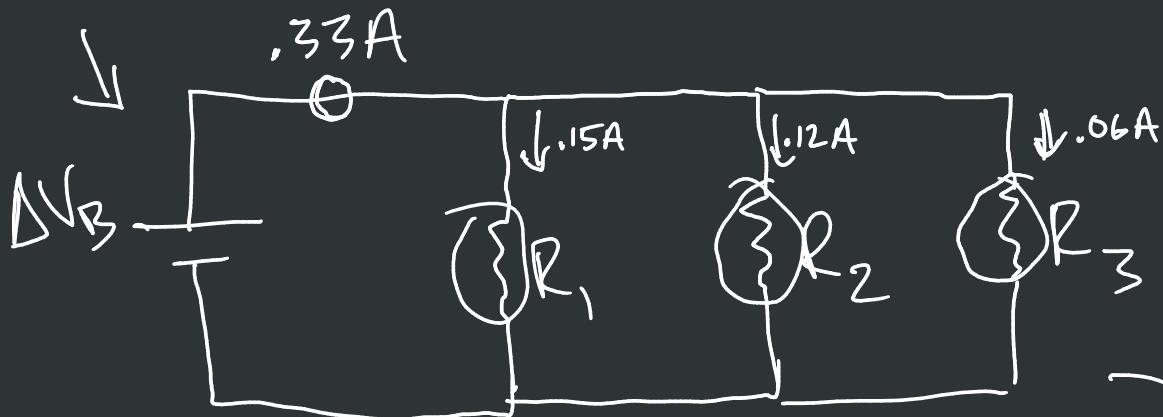
$$I_3 = \frac{V}{R_3} = \frac{12V}{200\Omega} = 0.06A$$



For resistors in parallel

$$R_E = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$$

$$\Rightarrow R_E = \frac{1}{\frac{1}{80} + \frac{1}{100} + \frac{1}{200}}$$

$$= \frac{1}{.0125 + .01 + .005}$$

$$= \frac{1}{.0275}$$

$$I_b = \frac{12V}{36.36\Omega} \quad \leftarrow \boxed{R_E = 36.36\Omega}$$


$$= 0.33A$$

Power → rate at which work is done/energy changes

$$\text{Power} = \frac{\text{Energy dissipated/used}}{\text{time it is on}}$$

$\left[ \frac{\text{Joule}}{\text{second}} \right]$ 
 $\left[ \frac{\text{Joule}}{\text{Coulomb}} \cdot \frac{\text{Coulomb}}{\text{second}} \right]$

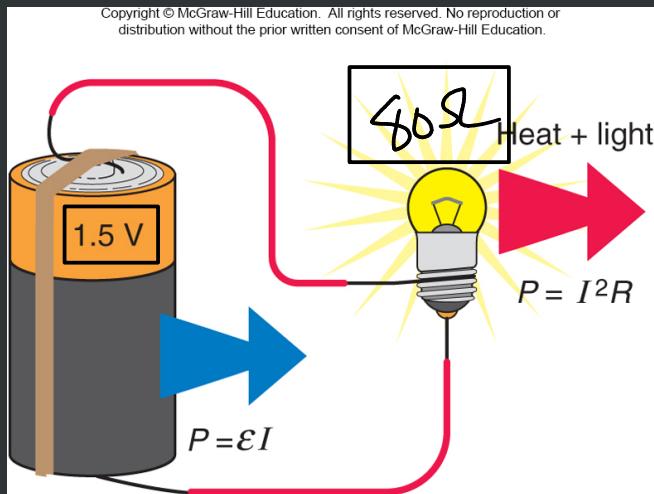Copyright © McGraw-Hill Education. All rights reserved. No reproduction or distribution without the prior written consent of McGraw-Hill Education.



$[\text{Watt}]$   $[\text{horsepower}]$

746 Watts = 1 horsepower

$$\text{Power} = \frac{\text{Voltage} \cdot \text{Current}}{}$$


$$\rightarrow P = V \cdot I = \frac{V^2}{R}$$

•  $P = V \cdot I$

(best) •  $P = \frac{V^2}{R}$

$$\text{Ohm's} \rightarrow R = \frac{V}{I} \Rightarrow I = \frac{V}{R}$$

$$\bullet P = I^2 R$$

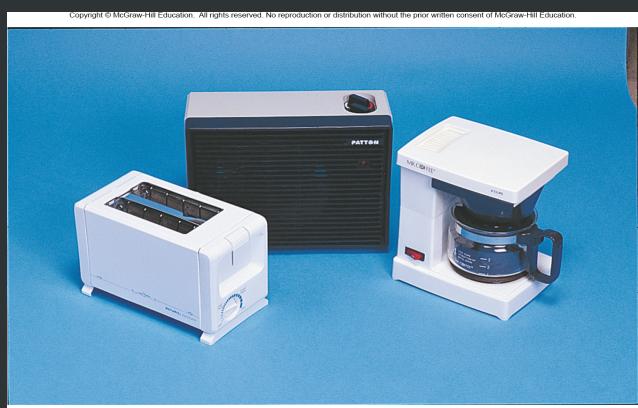

$$P = 100 \text{ Watts}$$

$$V = 120 \text{ Volts}$$

$$R = ?$$

$$I = ?$$

$$P = \frac{V^2}{R}$$

$$100W = \frac{(120V)^2}{R}$$

$$R = \frac{120^2}{100} = 144 \Omega$$


$$P = V \cdot I$$

$$100W = 120V \cdot I$$

$$I = \frac{100W}{120V}$$

$$I = .83A$$

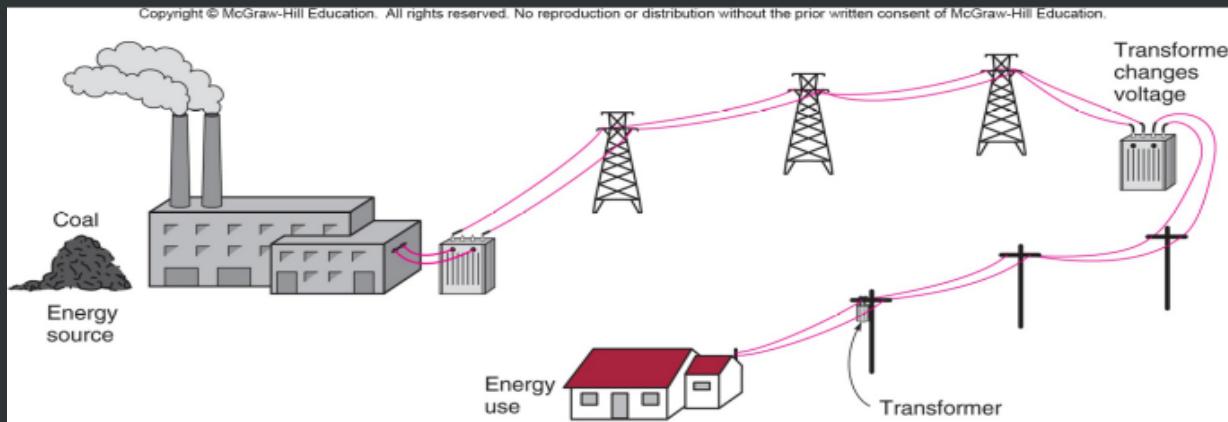Copyright © McGraw-Hill Education. All rights reserved. No reproduction or distribution without the prior written consent of McGraw-Hill Education.



Kilowatt-hours

1600 watt-hours

power . time

$$P = \frac{E}{t} \Rightarrow \text{Energy} = \underline{\text{power}} \cdot \underline{\text{time}}$$

Copyright © McGraw-Hill Education. All rights reserved. No reproduction or distribution without the prior written consent of McGraw-Hill Education.


table 13.2



Power and Current Ratings of Some Common Appliances

Appliance	Power (W)	Current (A)
stove	6000 (220 V)	27
clothes dryer	5400 (220 V)	25
water heater	4500 (220 V)	20
clothes washer	1200	10
dishwasher	1200	10
electric iron	1100	9
coffeemaker	1000	8
toaster	850	7
hair dryer	650	5
food processor	500	4
large fan	240	2
color television	100	0.8
small fan	50	0.4
personal computer	45	0.4
clock radio	12	0.1

These values vary, depending on the size and design of a particular appliance.

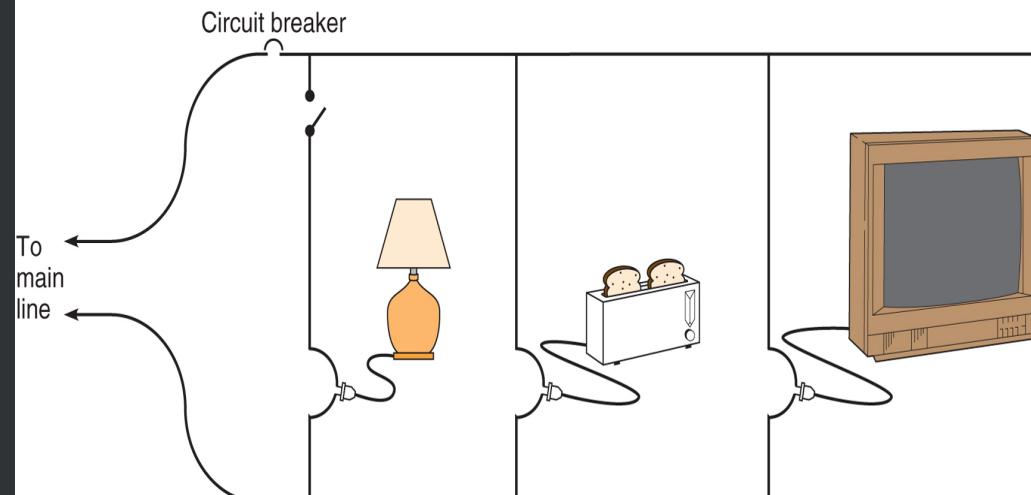Copyright © McGraw-Hill Education. All rights reserved. No reproduction or distribution without the prior written consent of McGraw-Hill Education.



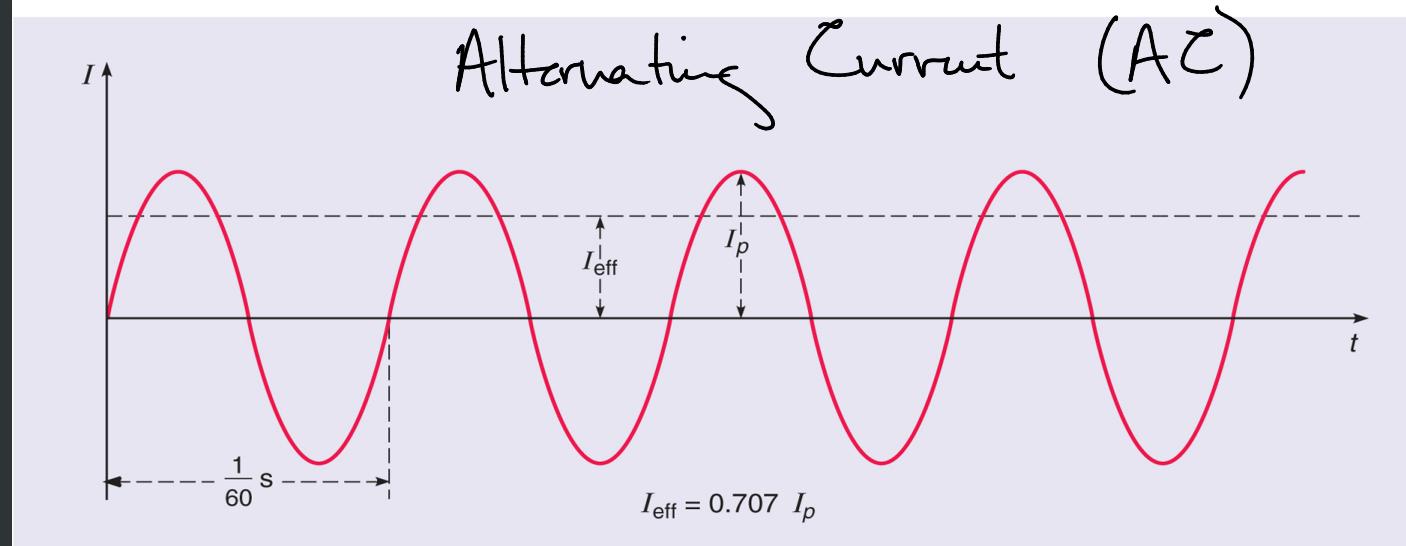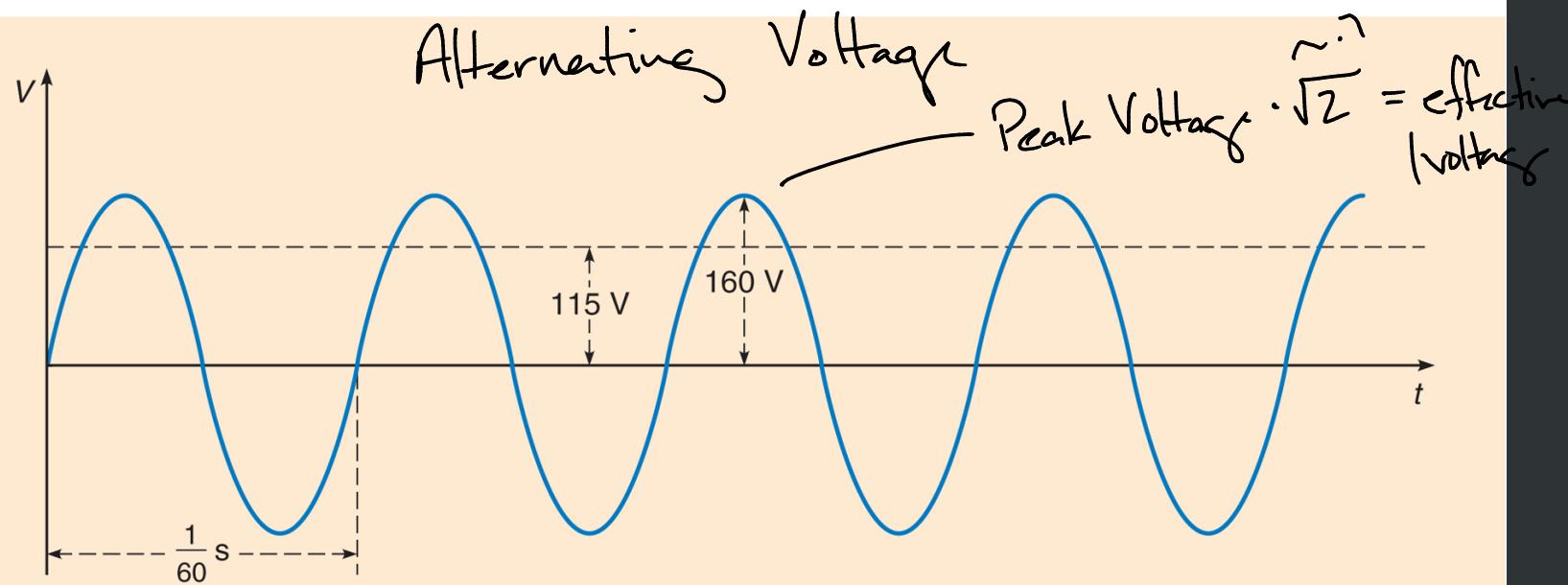

1)  $Q = 28C$  → passing through a resistor  
    amount that passes in 7 seconds

$$I = ? \quad I = \frac{Q}{t} = \frac{28C}{7s} = \underline{4 \text{ Amps}}$$

2) A current of 4.5A flows for 3 minutes  
How much charge passes?

$$\underbrace{I = \frac{Q}{t}}_{4.5 \text{ Amps}} \Rightarrow Q = I \cdot t = 4.5A \cdot 180 \text{ seconds} = 810C$$

    3 min → 180 seconds



# 13-14

$$P = I \cdot V$$

$$30W = I \cdot 80V$$

$$I = \frac{P}{V} = \frac{30W}{80V} = .375 A$$

---

$$V = I R$$

$$80V = .375A \cdot R$$

$$R = \frac{V}{I} = \frac{80V}{.375A} = 213 \Omega$$

---

$$60W \rightarrow I = ?$$

$$60W = I \cdot 80V \quad \leftarrow \text{brighter!}$$

$$I = \frac{60}{80} = \underline{\underline{.75A}}$$

$$80V = .75A \cdot R$$

$$\frac{80}{.75} = R = \underline{\underline{106.7 \Omega}}$$

lower  $R$   
than the 30W  
bulb!